



Optimized Implementation of Logic Functions

Chapter 4



Chapter Objectives



- ▶ Synthesis of logic functions
- ▶ Analysis of logic circuits
- ▶ Techniques for deriving minimum-cost implementation of logic functions
- ▶ Graphical representation of logic functions in the form of Karnaugh maps





Contents



1. Karnaugh Map
2. Strategy for Minimization
3. Minimization of POS Forms
4. Incompletely Specified Function
5. Multiple-Output Circuits
6. Multilevel Synthesis
7. Analysis of Multilevel Circuits





KARNAUGH MAP





Why Karnaugh Map?



Table 2-2
Truth Tables for F_1 and F_2

x	y	z	F_1	F_2	
0	0	0	0	0	
0	0	1	1 (1)	1	
0	1	0	0	0	
0	1	1	0	1	(1) : (3)
1	0	0	1 (2)	1	(2) : (3), (4)
1	0	1	1 (3)	1	(3) : (1), (5)
1	1	0	1 (4)	0	(4) : (2), (5)
1	1	1	1 (5)	0	(5) : (3), (4)

$$F_1 = \underset{(1)}{x'y'z} + \underset{(2)}{xy'z'} + \underset{(3)}{xy'z} + \underset{(4)}{xyz'} + \underset{(5)}{xyz}$$



Minimization by Boolean Functions

$$\begin{aligned} F_1 &= \overset{(1)}{x'y'z} + \overset{(2)}{xy'z'} + \overset{(3)}{xy'z} + \overset{(4)}{xyz'} + \overset{(5)}{xyz} && (1)+(3), (2)+(3), (4)+(5) \\ &= y'z(x' + x) + xy'(z' + z) + xy(z' + z) && \begin{array}{l} x + x = x \\ x + x' = 1 \end{array} \\ &= y'z + xy' + xy \\ &= x(y' + y) + y'z = \boxed{x + y'z} \end{aligned}$$

$$\begin{aligned} F_1 &= \overset{(1)}{x'y'z} + \overset{(2)}{xy'z'} + \overset{(3)}{xy'z} + \overset{(4)}{xyz'} + \overset{(5)}{xyz} && (1)+(3), (2)+(4), (4)+(5) \\ &= y'z(x' + x) + xz'(y' + y) + xy(z' + z) \\ &= \boxed{y'z + xz' + xy} \end{aligned}$$



Why Karnaugh Map?



- ▶ How can we **find minimum cost** expression?
- ▶ Is it **a unique optimal solution** for a given truth table?
- ▶ Are there any **strategies or procedures** for the minimum cost implementation?



Karnaugh Map

$$m_0 + m_4 = ?$$

$$m_2 + m_6 = ?$$

$$f = x'_3 + x_1 x'_2$$

Row number	x_1	x_2	x_3	f
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$m_0 + m_2 = x'_1 x'_2 x'_3 + x'_1 x_2 x'_3$$

$$= x'_1 x'_3 (x'_2 + x_2)$$

$$= x'_1 x'_3$$

$$m_4 + m_6 = x_1 x'_2 x'_3 + x_1 x_2 x'_3$$

$$= x_1 x'_3 (x'_2 + x_2)$$

$$= x_1 x'_3$$

$$x'_1 x'_3 + x_1 x'_3 = x'_3$$

$$m_4 + m_5 = x_1 x'_2 x'_3 + x_1 x'_2 x_3$$

$$= x_1 x'_2 (x'_3 + x_3)$$

$$= x_1 x'_2$$

Figure 4.1. The function $f(x_1, x_2, x_3) = \sum (0, 2, 4, 5, 6)$.

Karnaugh Map

	x_1	x_2	x_3
m_4	1	0	0
m_5	1	0	1

$$m_4 + m_5 = x_1 x'_2 (x'_3 + x_3)$$

$$x_3 = 0 \quad 1$$

	x_1	x_2	x_3
m_0	0	0	0
m_2	0	1	0
m_4	1	0	0
m_6	1	1	0

$$m_0 + m_2 = x'_1 x'_3 (x'_2 + x_2)$$

$$m_4 + m_6 = x_1 x'_3 (x'_2 + x_2)$$

$$x_2 = 0 \quad 1$$

$$x'_3$$

$$x_1$$


$$0$$

$$1$$

Two-Variable Map

x_1	x_2	f	
0	0	m_0	$m_0 = x'_1 x'_2$
0	1	m_1	$m_1 = x'_1 x_2$
1	0	m_2	$m_2 = x_1 x'_2$
1	1	m_3	$m_3 = x_1 x_2$

(a) Truth table

 


(b) Karnaugh map

Figure 4.2. Location of two-variable minterms.

Two-Variable Map

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

Figure 2.15

 

$$\begin{aligned}
 x_2 &= m_1 + m_3 \\
 &= x_1' x_2 + x_1 x_2 \\
 &= x_2 (x_1' + x_1) \\
 &\quad \text{where } x_1' = 0 \text{ and } x_1 = 1
 \end{aligned}$$


$$\begin{aligned}
 x_1' &= m_0 + m_1 \\
 &= x_1' x_2' + x_1' x_2 \\
 &= x_1' (x_2' + x_2) \\
 &\quad \text{where } x_2' = 0 \text{ and } x_2 = 1
 \end{aligned}$$

Figure 4.3. The function of Figure 2.15.

Three-Variables Map

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

(a) Truth table

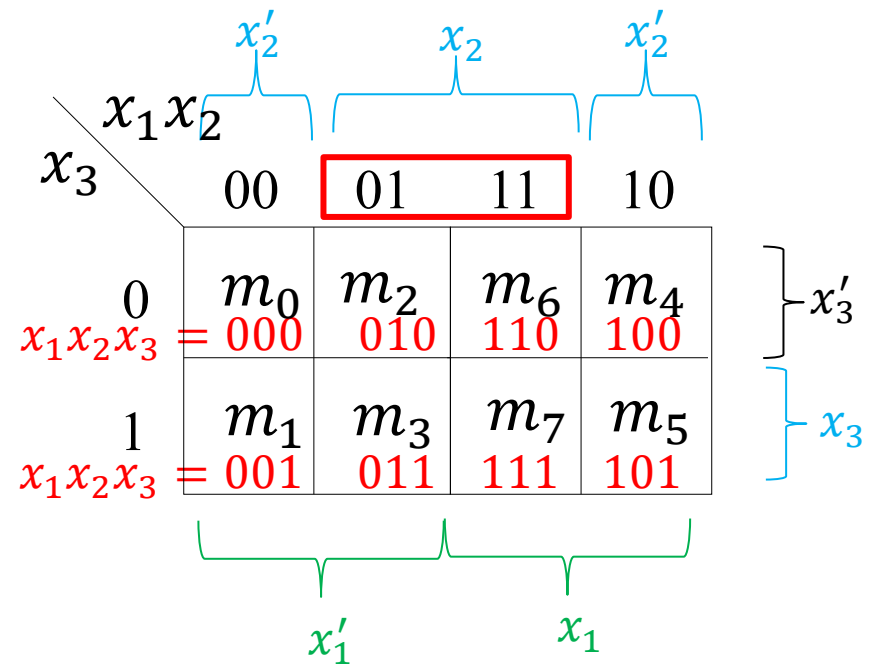


(b) Karnaugh map

Figure 4.4. Location of three-variable minterms.

Row number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Figure 2.18

 

(a) The function of Figure 2.18

$$xy + x'z + yz = xy + x'z$$

$$yz(x' + x) \quad xy(1 + z)$$

$$x_3x'_2 + x'_3x_1 + x'_2x_1 = x_3x'_2 + x'_3x_1$$

$$\text{let } x = x_3, y = x'_2, z = x_1$$

Figure 4.5. Examples of three-variable Karnaugh maps.


Row number	x_1	x_2	x_3	f
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Figure 4.1

$$\begin{aligned}
 m_0 + m_2 &= x_1' x_2' x_3' + x_1' x_2 x_3' \\
 &= x_1' x_3' (x_2' + x_2) \\
 &= x_1' x_3'
 \end{aligned}$$

$$\begin{aligned}
 m_4 + m_6 &= x_1 x_2' x_3' + x_1 x_2 x_3' \\
 &= x_1 x_3' (x_2' + x_2) \\
 &= x_1 x_3'
 \end{aligned}$$

$$x_1' x_3' + x_1 x_3' = x_3'$$

 

(b) The function of Figure 4.1

Figure 4.5. Examples of three-variable Karnaugh maps.

Four-Variables Map

 


Figure 4.6. A four-variable Karnaugh map.

 


Figure 4.7. Examples of four-variable Karnaugh maps.

 


Figure 4.7. Examples of four-variable Karnaugh maps.

 


Figure 4.7. Examples of four-variable Karnaugh maps.

 


Figure 4.7. Examples of four-variable Karnaugh maps.

Five-Variables Map

 


Figure 4.8. A five-variable Karnaugh map.



STRATEGY FOR MINIMIZATION





Terminology



- ▶ **Literal:** Each appearance of a variables is called a literal
- ▶ **Implicant:** A product term that indicates the input valuation(s) for which a given function is equal to 1 is called an implicant of the function
- ▶ **Prime implicant:** An implicant is called a prime implicant if it cannot be combined into another implicant that has fewer literals
- ▶ **Cover:** A collection of implicants that accounts for all variations for which a given function is equal to 1 is called a cover for that function
- ▶ **Cost:** The number of gates + the total number of input to all gates

Literal and Implicant

Literal

$x_1 x_2' x_3$: 3 literals

$x_1' x_3 x_4' x_6$: 4 literals

Implicant

- Basic implicant: minterm
- Implicants of Figure 4.9: 11 implicants
 - 5 minterms (m_0, m_1, m_2, m_3, m_7)
 - 5 pairs of minterms ($m_0 + m_1, m_0 + m_2, m_1 + m_3, m_2 + m_3, m_3 + m_7$)
 - 1 implicant of 4 minterms ($m_0 + m_1 + m_2 + m_3$)

 


Figure 4.9. Three-variable function $f(x_1, x_2, x_3) = \sum m(0, 1, 2, 3, 7)$.

○○○ Prime Implicant and Cover ○○○

Prime Implicants

➤ x_1' and x_2x_3

Cover

$$f = \sum (0,1,2,3,7)$$

$$f = x_1'x_2' + x_1'x_2 + x_2x_3$$

$$f = x_1' + x_2x_3$$

 


Figure 4.9. Three-variable function $f(x_1, x_2, x_3) = \sum m(0, 1, 2, 3, 7)$.



Cover and Cost



Cover

Cost

$$f = \sum (0,1,2,3,7)$$

Canonical SOP form

5 x 3-input AND, 1 x 5-input OR
: 6 gates + 20 inputs = **26**

$$f = x_1'x_2' + x_1'x_2 + x_2x_3$$

3 x 2-input AND, 1 x 3-input OR
: 4 gates + 9 = **13**

$$f = x_1' + x_2x_3$$


Optimal Solution !!!

1 x 2-input AND, 1 x 2-input OR
: 2 gates + 4 inputs = **6**



○○○ Minimization Procedure ○○○

 
1. Generate **all prime implicants** for the given function f
2. Find the set of **essential prime implicants**
3. If the set of essential prime implicants covers all valuations for $f = 1$, then this set is the desired cover of f .



$$f = x_2'x_3 + x_3x_4' + x_2x_3'x_4 + x_1'x_3$$

$x_1'x_2x_4$

Figure 4.10. Four-variable function $f(x_1, \dots, x_4) = \Sigma m(2, 3, 5, 6, 7, 10, 11, 13, 14)$.

 

$$f = x_3'x_4' + x_1x_2x_4 + x_1x_2'x_3$$

Figure 4.11. The function $f(x_1, \dots, x_4) = \sum m(0, 4, 8, 10, 11, 12, 13, 15)$.

Cost

- 4 x 3-input AND
- 1 x 4-input OR
- $4 + (4 \times 3 + 1 \times 4) = 20$

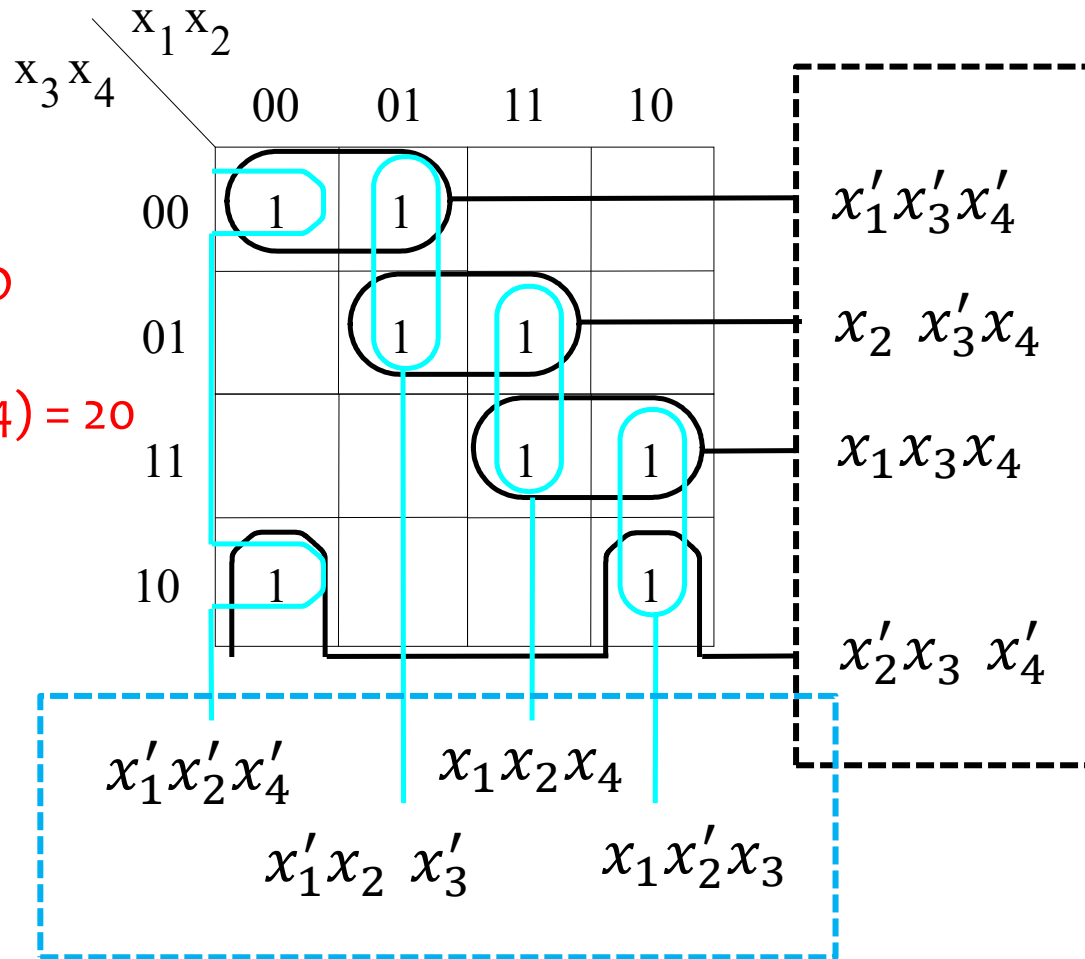


Figure 4.12. The function $f(x_1, \dots, x_4) = \sum m(0, 2, 4, 5, 10, 11, 13, 15)$.



MINIMIZATION OF PRODUCT-OF-SUMS FORMS



Minimization of POS Forms

$$x + yz = (x + y)(x + z)$$

$x_1 x_2$		00	01	11	10
x_3	0	1	1	0	0
	1	1	1	1	0

$(x'_1 + x_3)$ M_6 M_4
 $= (x'_1 + x'_2 + x_3)(x'_1 + x_2 + x_3)$
 $= (x'_1 + x_3 + x'_2)(x'_1 + x_3 + x_2)$
 $= (x'_1 + x_3) + x'_2 x_2$


$(x'_1 + x_2)$ M_5 M_4
 $= (x'_1 + x_2 + x'_3)(x'_1 + x_2 + x_3)$
 $= (x'_1 + x_2) + x'_3 x_3$

$$f = (x'_1 + x_3)(x'_1 + x_2)$$

Figure 4.13. POS minimization of $f(x_1, x_2, x_3) = \Pi M(4, 5, 6)$.



Minimization of POS Forms

 

$$f = (x_3 + x_4)(x_2 + x_3)(x'_1 + x'_2 + x'_3 + x'_4)$$

Figure 4.14. POS minimization of $f(x_1, \dots, x_4)$
 $= \Pi M(0, 1, 4, 8, 9, 12, 15)$.



INCOMPLETELY SPECIFIED FUNCTION



○○ Incompletely Specified Function ○○


Don't care term : d

x_1	x_2	x_3	x_4	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0

x_1	x_2	x_3	x_4	f
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	d
1	1	0	1	d
1	1	1	0	d
1	1	1	1	d

Figure 4.15. Two implementations of the function $f(x_1, \dots, x_4) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$

○○ Incompletely Specified Function ○○

 

(a) **SOP** implementation

Figure 4.15. Two implementations of the function $f(x_1, \dots, x_4) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$.

○○ Incompletely Specified Function ○○

$$f = (x_2 + x_3)(x_1 + x'_3 + x'_4)(x_2 + x'_3 + x'_4) \quad \text{Without don't care terms}$$

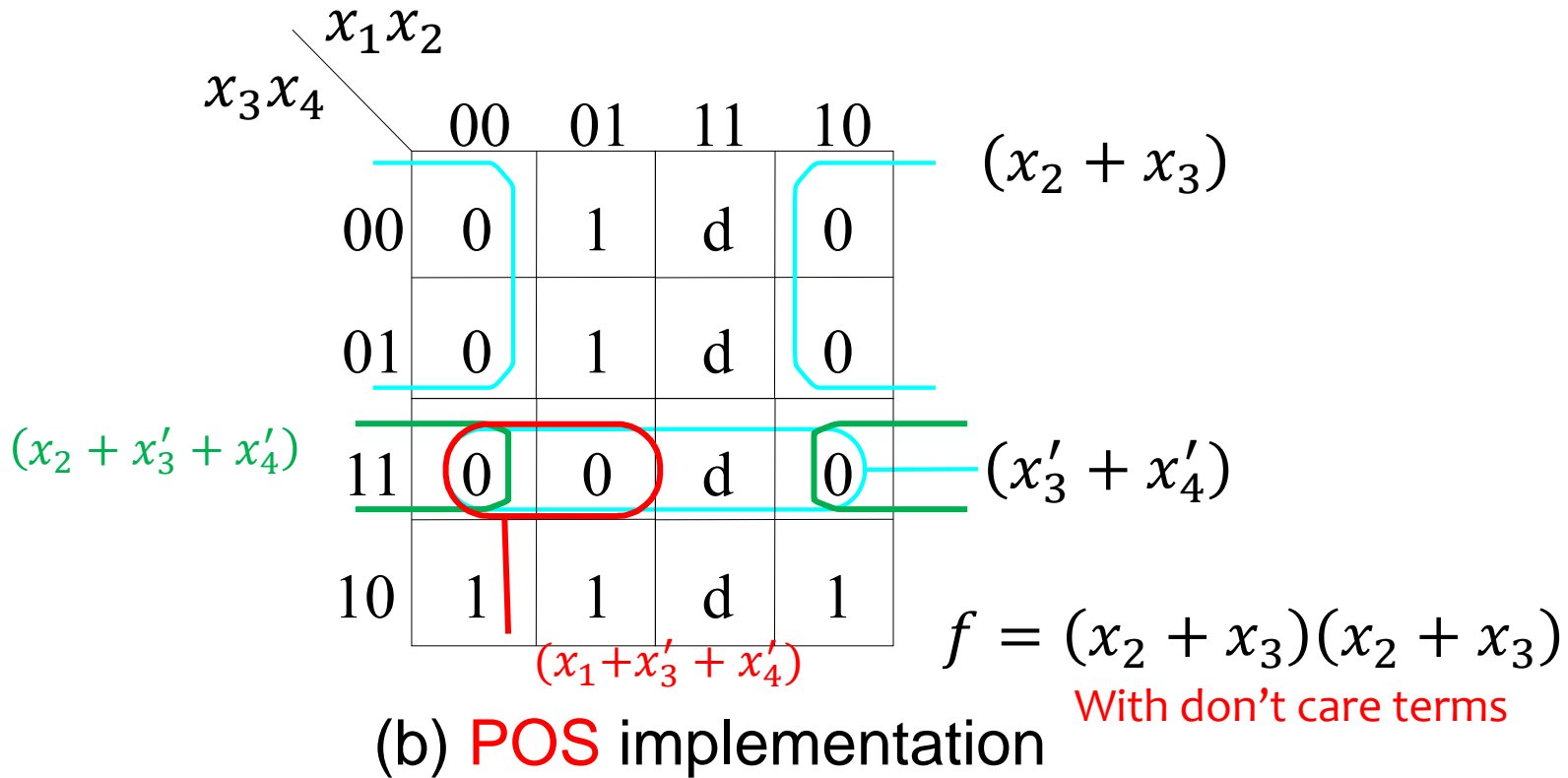


Figure 4.15. Two implementations of the function $f(x_1, \dots, x_4) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$.



MULTIPLE-OUTPUT CIRCUITS



Multiple-Output Circuits


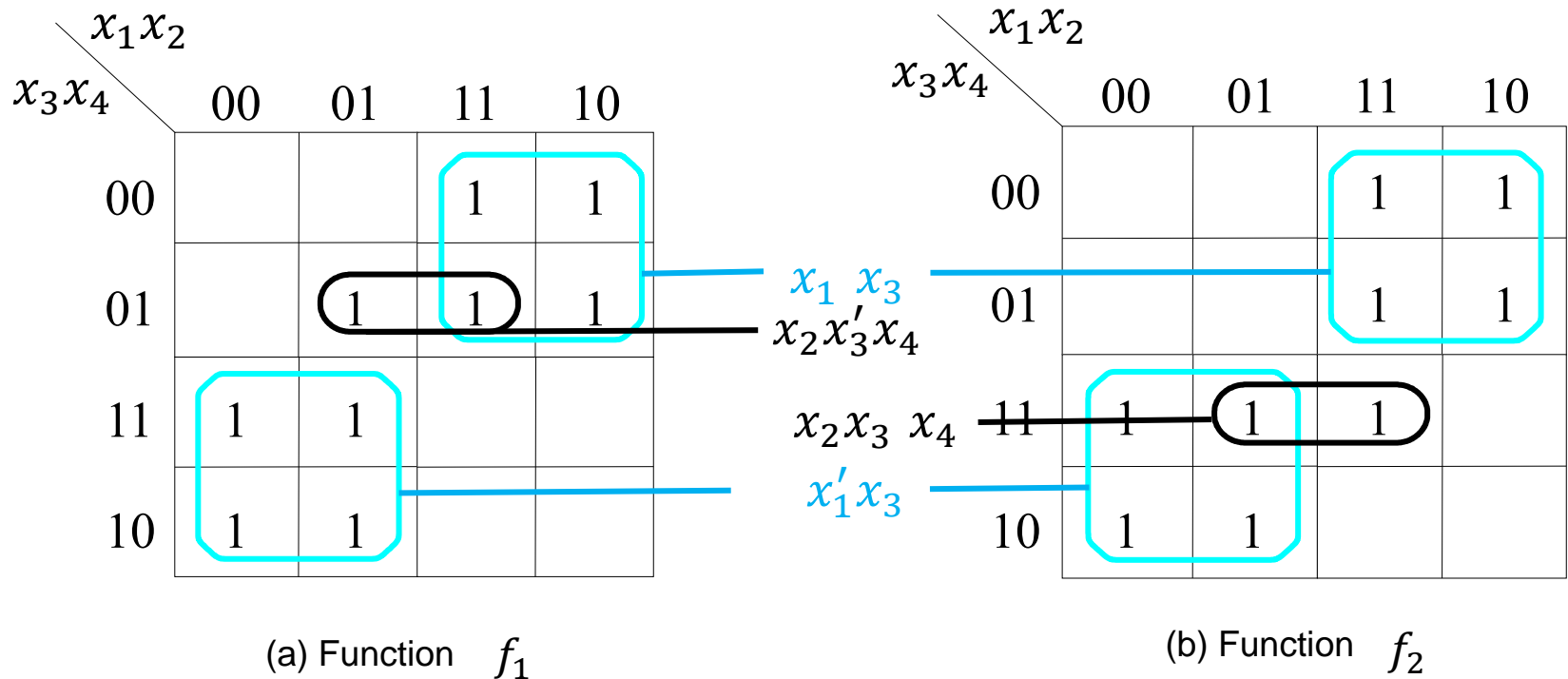



Figure 4.16. An example of multiple-output synthesis.

Multiple-Output Circuits

 


(c) Combined circuit for f_1 and f_2

Figure 4.16. An example of multiple-output synthesis.

 



(a) Optimal realization of f_3

 

(b) Optimal realization of f_4

$$f_3 = x_2x_4 + x_1'x_4 + x_1'x_2x_3 \quad f_4 = x_1x_4 + x_2'x_4 + x_1'x_2x_3x_4'$$

Figure 4.17. An example of multiple-output synthesis.

  


$$f_3 = x_1x_2x_4 + x_1'x_4 + x_1'x_2x_3x_4'$$

$$f_4 = x_1x_2x_4 + x_2'x_4 + x_1'x_2x_3x_4'$$

(c) Optimal realization of f_3 and f_4 together

Figure 4.17. An example of multiple-output synthesis.

 

(d) Combined circuit for f_3 and f_4

Figure 4.17. An example of multiple-output synthesis.



Cost for Multiple-Output



$$f_3 = x_2x_4 + x'_1x_4 + x'_1x_2x_3$$

Cost for f_3

- 2 x 2-input ANDs, 1 x 3-input AND, 1 x 3-input OR
- $4 + (2 \times 2 + 1 \times 3 + 1 \times 3) = 14$

$$f_4 = x_1x_4 + x'_2x_4 + x'_1x_2x_3x'_4$$

Cost for f_4

- 2 x 2-input ANDs, 1 x 4-input AND, 1 x 3-input OR
- $4 + (2 \times 2 + 1 \times 4 + 1 \times 3) = 15$

Total cost : $14 + 15 = 29$





Cost for Multiple-Output



$$f_3 = x_1x_2x_4 + x_1'x_4 + x_1'x_2x_3x_4'$$

Cost for f_3

- 1 x 2-input AND, 1 x 3-input AND, 1 x 4-input AND, 1 x 3-input OR
- $4 + (1 \times 2 + 1 \times 3 + 1 \times 4 + 1 \times 3) = 16$

$$f_4 = x_1x_2x_4 + x_2'x_4 + x_1'x_2x_3x_4'$$

Cost for f_4

- 1 x 2-input AND, 1 x 3-input AND, 1 x 4-input AND, 1 x 3-input OR
- $4 + (1 \times 2 + 1 \times 3 + 1 \times 4 + 1 \times 3) = 16$

Cost for f_3 and f_4 together

- 2 x 2-input ANDs, 1 x 3-input AND, 1 x 4-input AND, 2 x 3-input OR
- $6 + (2 \times 2 + 1 \times 3 + 1 \times 4 + 2 \times 3) = 23$

$$\text{Total cost : } 16 + 16 - 9 = 23$$

$$\frac{(29-23)}{29} \times 100 \% = 21\%$$



MULTILEVEL SYNTHESIS






Multilevel Synthesis



- ▶ Fan-in problem
 - ▶ Limited number of inputs
 - ▶ Fan-out problem: Limited number of outputs
- ▶ Implementation
 - ▶ CPLD: two-level logic expression (Sum of Products)
 - ▶ FPGA: multilevel logic expression
- ▶ Two Important Techniques for Synthesis of Multilevel Circuits
 - ▶ Factoring
 - ▶ Functional Decomposition



Standard SOP form

 

$$f(x_1, \dots, x_7) = x_1x_3x_6' + x_1x_4x_5x_6' + x_2x_3x_7 + x_2x_4x_5x_7$$

Figure 4.18. Implementation in a CPLD.



4-to-1 Multiplexer, LUT (Look Up Table), Logic Cell



 
 
 
 
 


Figure 4.19. Implementation in an FPGA.

 

LUT operation

 

Factoring

$$f = x_1x'_6(x_3 + x_4x_5) + x_2x_7(x_3 + x_4x_5)$$

2 x 3-input ANDs, 2 x 2-input ANDs, 3 x 2-input OR

In the previous slide, the circuit has a maximum fan-in of two, 2-input LUTs

By the distributive property,

$$f = (x_3 + x_4x_5)(x_1x'_6 + x_2x_7)$$

4 x 2-input ANDs, 2 x 2-input ORs



Factoring



$$f = x_1x_2x_3x_4x_5x_6x_7 = (x_1x_2x_3x_4)x_5x_6x_7$$

1 x 7 input AND = 2 x 4-input ANDs

If Fan-in : Max. 4

 


Figure 4.20. Using four-input AND gates to realize a seven-input product term.

$$f = x_1 x_2' x_3 x_4' x_5 x_6 + x_1 x_2 x_3' x_4' x_5' x_6$$

2 x 6-input ANDs, 1 x 2-input OR

If Fan-in : Max. 4

$$f = x_1 x_4' x_6 (x_2' x_3 x_5 + x_2 x_3' x_5')$$

 


Figure 4.21. A factored circuit.

Example 4.5

For four input system, x_1, x_2, x_3 and x_4

(1) $f_1 = 1$ if at least one of x_1 and $x_2 = 1$,
both x_3 and $x_4 = 1$;

$$(x_1 + x_2)x_3x_4$$

$f_1 = 1$ if $x_1 = x_2 = 0$ and either x_3 or $x_4 = 1$

$$x'_1x'_2(x_3 + x_4)$$

(2) $f_2 = 1$ in all cases except when both x_1 and $x_2 = 0$
or when both x_3 and $x_4 = 0$

$$x'_1x'_2$$


$$x'_3x'_4$$

$$f_1 = (x_1 + x_2)x_3x_4 + x'_1x'_2(x_3 + x_4)$$

$$f'_2 = x'_1x'_2 + x'_3x'_4$$

$$f_2 = (x'_1x'_2 + x'_3x'_4)'$$

$$f_2 = (x_1 + x_2)(x_3 + x_4)$$

 

$$\begin{aligned}
 f_1 &= (x_1 + x_2)x_3x_4 + x_1'x_2'(x_3 + x_4) \\
 &= x_3x_4 + x_1'x_2'(x_3 + x_4) \\
 &= x_3x_4 + (x_1 + x_2)'(x_3 + x_4)
 \end{aligned}$$

Example 4.5

$$f_1 = x_3x_4 + (x_1 + x_2)'(x_3 + x_4)$$

$$f_2 = (x_1 + x_2)(x_3 + x_4)$$

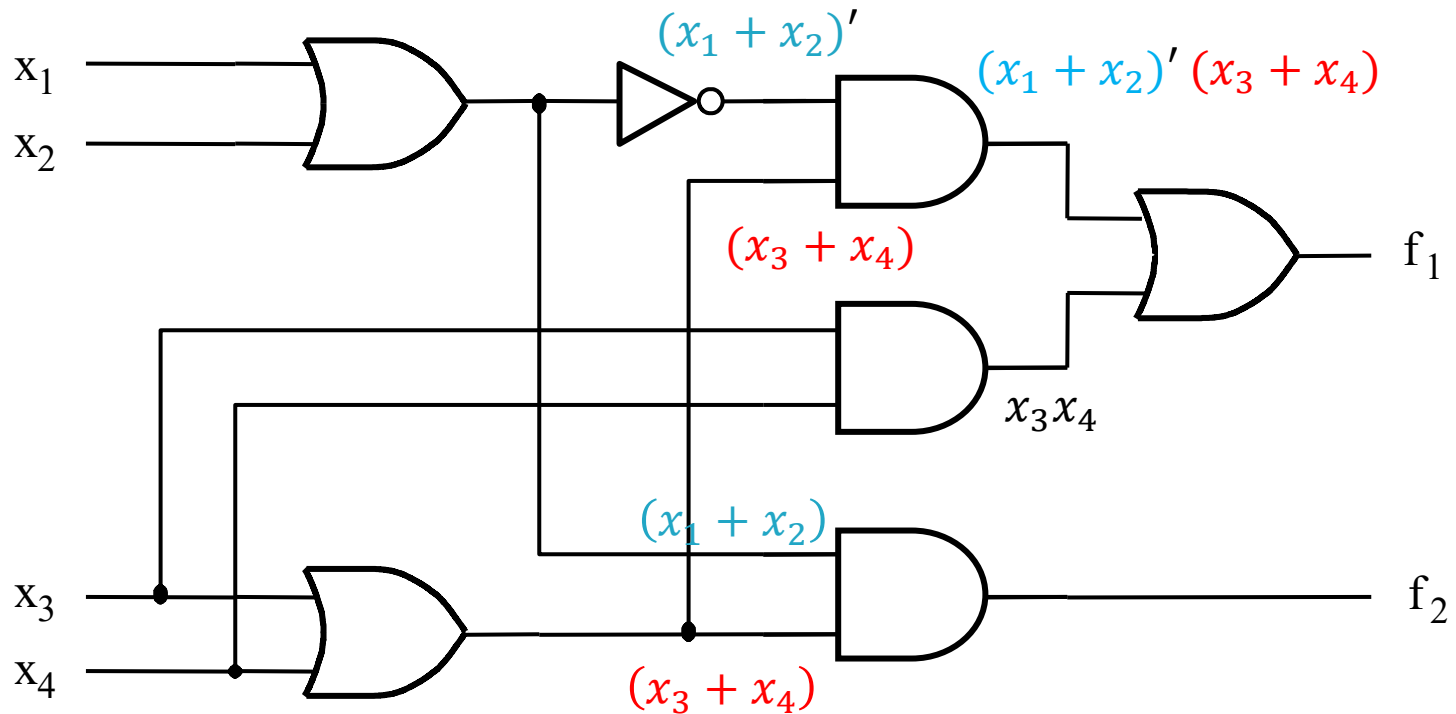


Figure 4.22. Circuit for Example 4.5.



Functional Decomposition



◆ Example 4.6

$$f = x_1'x_2x_3 + x_1x_2'x_3 + x_1x_2x_4 + x_1'x_2'x_4$$

- Minimum cost SOP expression
- 4 x 3-input ANDs, 1 x 4-input OR
- Cost: $5 + (4 \times 3 + 1 \times 4) = 21$

$$f = (x_1'x_2 + x_1x_2')x_3 + (x_1x_2 + x_1'x_2')x_4$$

$$g(x_1, x_2) = x_1'x_2 + x_1x_2' \quad \text{X-OR}$$

$$g'(x_1, x_2) = x_1x_2 + x_1'x_2' \quad \text{X-NOR}$$

- 6 x 2-input ANDs, 3 x 2-input OR
- Cost: $9 + (6 \times 2 + 3 \times 2) = 27$

$$f = gx_3 + g'x_4$$

- 4 x 2-input ANDs, 2 x 2-input OR
- Cost: $6 + (4 \times 2 + 2 \times 2) = 18$


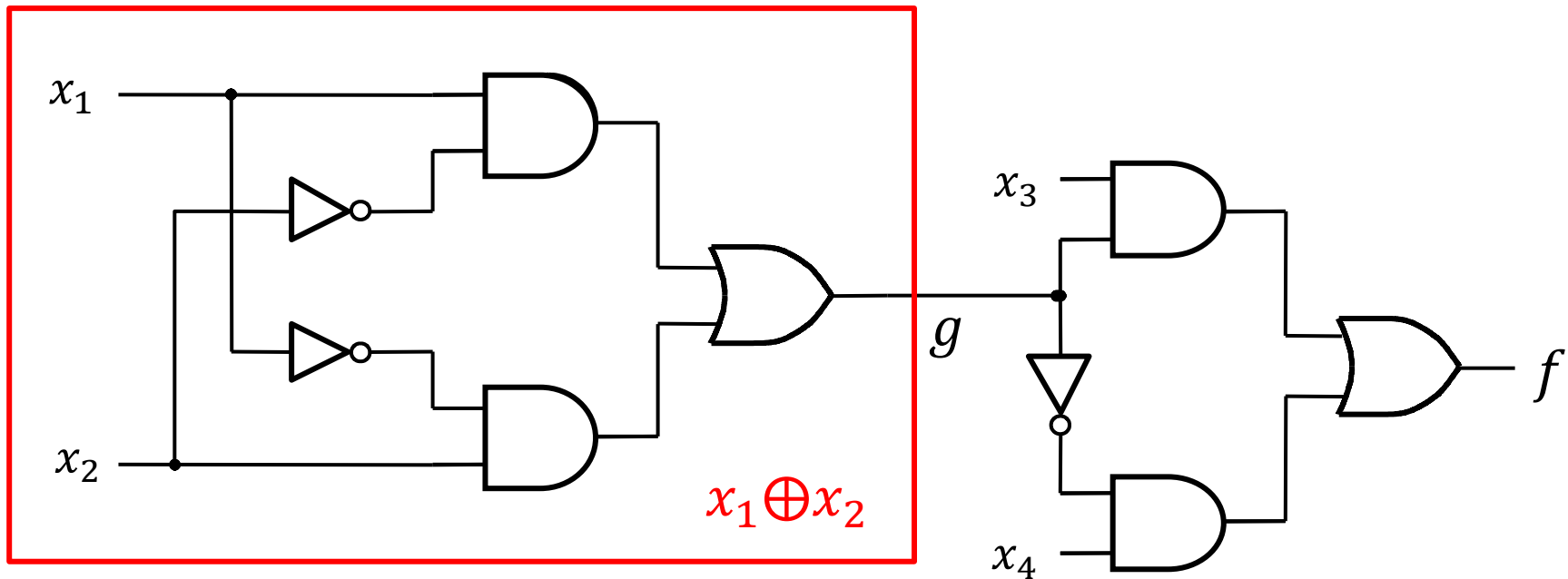
 


Figure 4.23. Logic circuit for Example 4.6.

 

$$f(x_1, x_2, x_3, x_4) = h[g(x_1, x_2), x_3, x_4]$$

Figure 4.24. The structure of decomposition in Example 4.6.

Example 4.7

$x_3x_4 \backslash x_1x_2$

	00	01	11	10
$x_1'x_2'x_3'x_4'x_5'$ 00	1			
$x_2x_3'x_4$ 01		1	1	1
$x_1'x_2'x_3x_4x_5'$ 11	1			
$x_2x_3x_4'$ 10		1	1	1

$x_5 = 0$

$x_3x_4 \backslash x_1x_2$

	00	01	11	10
00				
$x_1x_3'x_4$ 01	1	1	1	1
11				
$x_1x_3x_4'$ 10	1	1	1	1


$x_5 = 1$

$$f = x_1x_3'x_4 + x_1x_3x_4' + x_2x_3'x_4 + x_2x_3x_4' + x_3'x_4x_5 + x_3x_4'x_5 + x_1'x_2'x_3'x_4'x_5' + x_1'x_2'x_3x_4x_5'$$

6 x 3-input ANDs, 2 x 5-input ANDs, 1 x 8-input OR

Cost: $9 + (6 \times 3 + 2 \times 5 + 1 \times 8) = 45$


Functional Decomposition

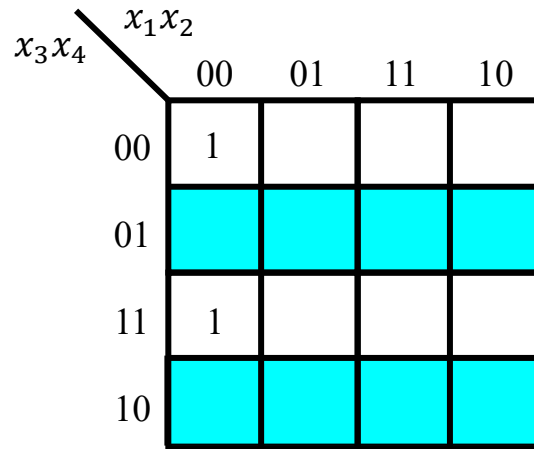

A 4x4 Karnaugh map for variables x_1, x_2, x_3, x_4 . The columns are labeled x_1x_2 as 00, 01, 11, 10. The rows are labeled x_3x_4 as 00, 01, 11, 10. The map shows 1s in the cells (00, 00), (00, 11), (01, 00), (01, 01), (01, 11), (01, 10), (11, 00), (11, 01), (11, 11), (11, 10), (10, 00), (10, 01), (10, 11), (10, 10). The cells (00, 00) and (00, 11) are white, while all other cells are cyan.

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00	1			
01				
11	1			
10				

$x_5 = 0$

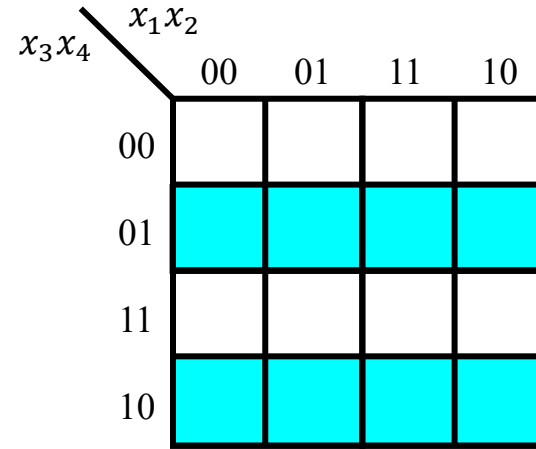


A 4x4 Karnaugh map for variables x_1, x_2, x_3, x_4 . The columns are labeled x_1x_2 as 00, 01, 11, 10. The rows are labeled x_3x_4 as 00, 01, 11, 10. The map shows 1s in the cells (01, 00), (01, 01), (01, 11), (01, 10), (11, 00), (11, 01), (11, 11), (11, 10), (10, 00), (10, 01), (10, 11), (10, 10). All cells are cyan.

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00				
01				
11				
10				

$x_5 = 1$


+

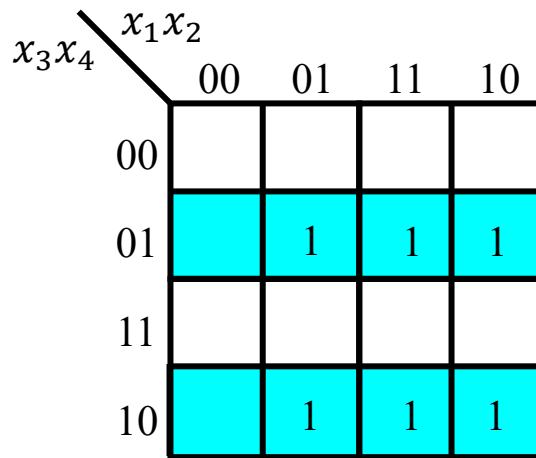

A 4x4 Karnaugh map for variables x_1, x_2, x_3, x_4 . The columns are labeled x_1x_2 as 00, 01, 11, 10. The rows are labeled x_3x_4 as 00, 01, 11, 10. The map shows 1s in the cells (01, 01), (01, 11), (01, 10), (11, 01), (11, 11), (11, 10), (10, 01), (10, 11), (10, 10). The cells (00, 01), (00, 11), (00, 10), (11, 00), (10, 00) are white, while all other cells are cyan.

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00				
01		1	1	1
11				
10		1	1	1

$x_5 = 0$

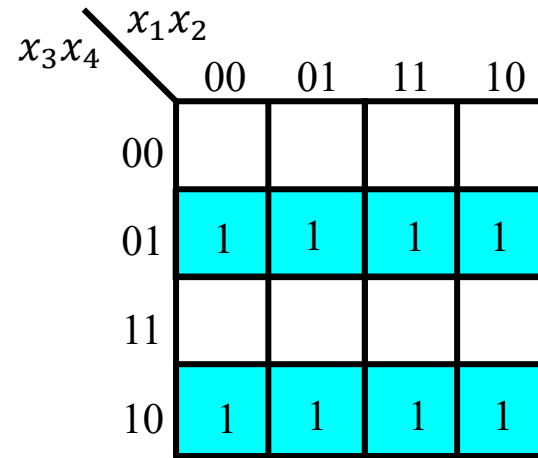

A 4x4 Karnaugh map for variables x_1, x_2, x_3, x_4 . The columns are labeled x_1x_2 as 00, 01, 11, 10. The rows are labeled x_3x_4 as 00, 01, 11, 10. The map shows 1s in the cells (01, 01), (01, 11), (01, 10), (11, 01), (11, 11), (11, 10), (10, 01), (10, 11), (10, 10). All cells are cyan.

$x_3x_4 \backslash x_1x_2$	00	01	11	10
00				
01		1	1	1
11				
10		1	1	1

$x_5 = 1$


$x_3x_4 \backslash x_1x_2$		x_1x_2			
		00	01	11	10
x_3x_4	00				
	01	1	1	1	1
	11				
	10	1	1	1	1

$x_5 = 0$


		x_1x_2			
		00	01	11	10
x_3x_4	00				
	01	1	1	1	1
	11				
	10	1	1	1	1

$x_5 = 1$
 
$$k = x_3'x_4 + x_3x_4' = x_3 \oplus x_4$$



$x_5 = 0$

 

x_1

x_2

x_5

$x_5 = 1$

$$g = x_1 + x_2 + x_5$$



		x_1x_2			
		00	01	11	10
x_3x_4	00				
	01	1	1	1	1
	11				
	10	1	1	1	1

$x_5 = 0$

		x_1x_2			
		00	01	11	10
x_3x_4	00				
	01	1	1	1	1
	11				
	10	1	1	1	1

$x_5 = 1$

k

AND

=

		x_1x_2			
		00	01	11	10
x_3x_4	00				
	01		1	1	1
	11				
	10		1	1	1

$x_5 = 0$

		x_1x_2			
		00	01	11	10
x_3x_4	00				
	01	1	1	1	1
	11				
	10	1	1	1	1

$x_5 = 1$

kg

		x_1x_2			
		00	01	11	10
x_3x_4	00		1	1	1
	01		1	1	1
	11		1	1	1
	10		1	1	1

$x_5 = 0$

		x_1x_2			
		00	01	11	10
x_3x_4	00	1	1	1	1
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1

$x_5 = 1$

g



$x_3x_4 \backslash x_1x_2$		00	01	11	10
		00	01	11	10
00		1	1	1	1
01					
11		1	1	1	1
10					

$x_5 = 0$

$x_3x_4 \backslash x_1x_2$		00	01	11	10
		00	01	11	10
00		1	1	1	1
01					
11		1	1	1	1
10					

$x_5 = 1$

k'

AND

=

$x_3x_4 \backslash x_1x_2$		00	01	11	10
		00	01	11	10
00		1			
01					
11		1			
10					

$x_5 = 0$

$x_3x_4 \backslash x_1x_2$		00	01	11	10
		00	01	11	10
00					
01					
11					
10					

$x_5 = 1$

$k'g'$

$x_3x_4 \backslash x_1x_2$		00	01	11	10
		00	01	11	10
00		1			
01		1			
11		1			
10		1			

$x_5 = 0$


$x_3x_4 \backslash x_1x_2$		00	01	11	10
		00	01	11	10
00					
01					
11					
10					

$x_5 = 1$

g'

Decomposition for Example 4.7

$$f = h[g(x_1, x_2, x_5), k(x_3, x_5)]$$

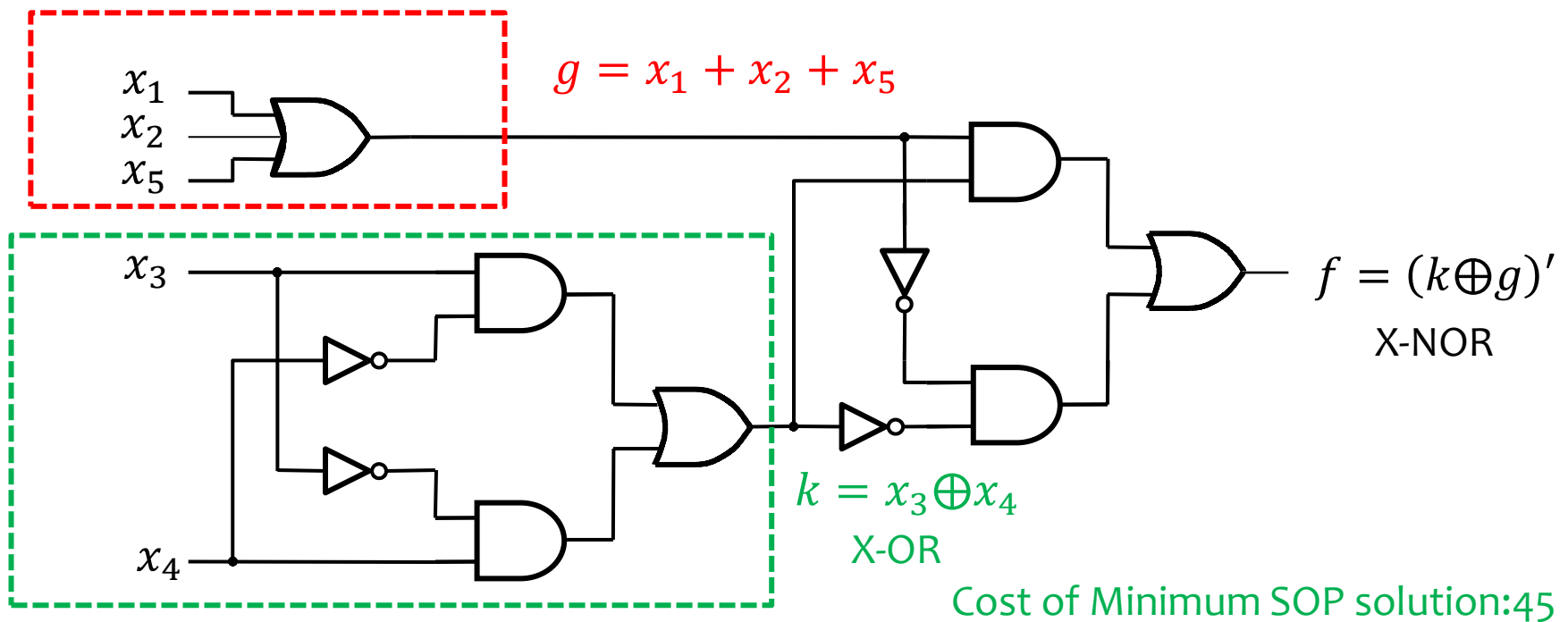


(b) Circuit obtained using decomposition

4 x 2-input ANDs, 2 x 2-input ORs, 1 x 3-input OR

Cost: $7 + (4 \times 2 + 2 \times 2 + 1 \times 3) = 22$

Implementation of XOR

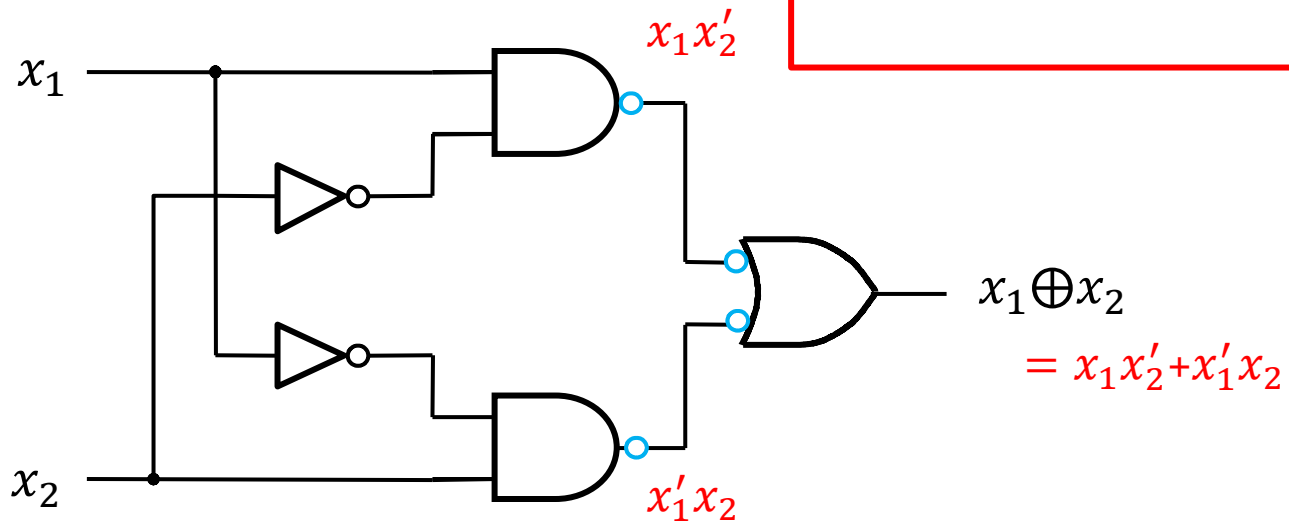


(a) Sum-of-products implementation

Figure 4.26. Implementation of XOR



Implementation of XOR

 


(b) NAND gate implementation

Figure 4.26. Implementation of XOR



Implementation of XOR

 


$$\begin{aligned} x_1 \oplus x_2 &= ((x_1' + x_2)(x_2' + x_1))' \\ &= (x_1'x_2' + x_1'x_1 + x_2'x_2 + x_1x_2)' \\ &= (x_1'x_2' + x_1x_2)' \quad \text{X-NOR} \end{aligned}$$

(c) Optimal NAND gate implementation

Figure 4.26. Implementation of XOR


○ ○ Multilevel NAND and NOR Circuits ○ ○

 

(a) Circuit with AND and OR gates

Figure 4.27. Conversion to a NAND-gate circuit.


Multilevel NAND and NOR Circuits

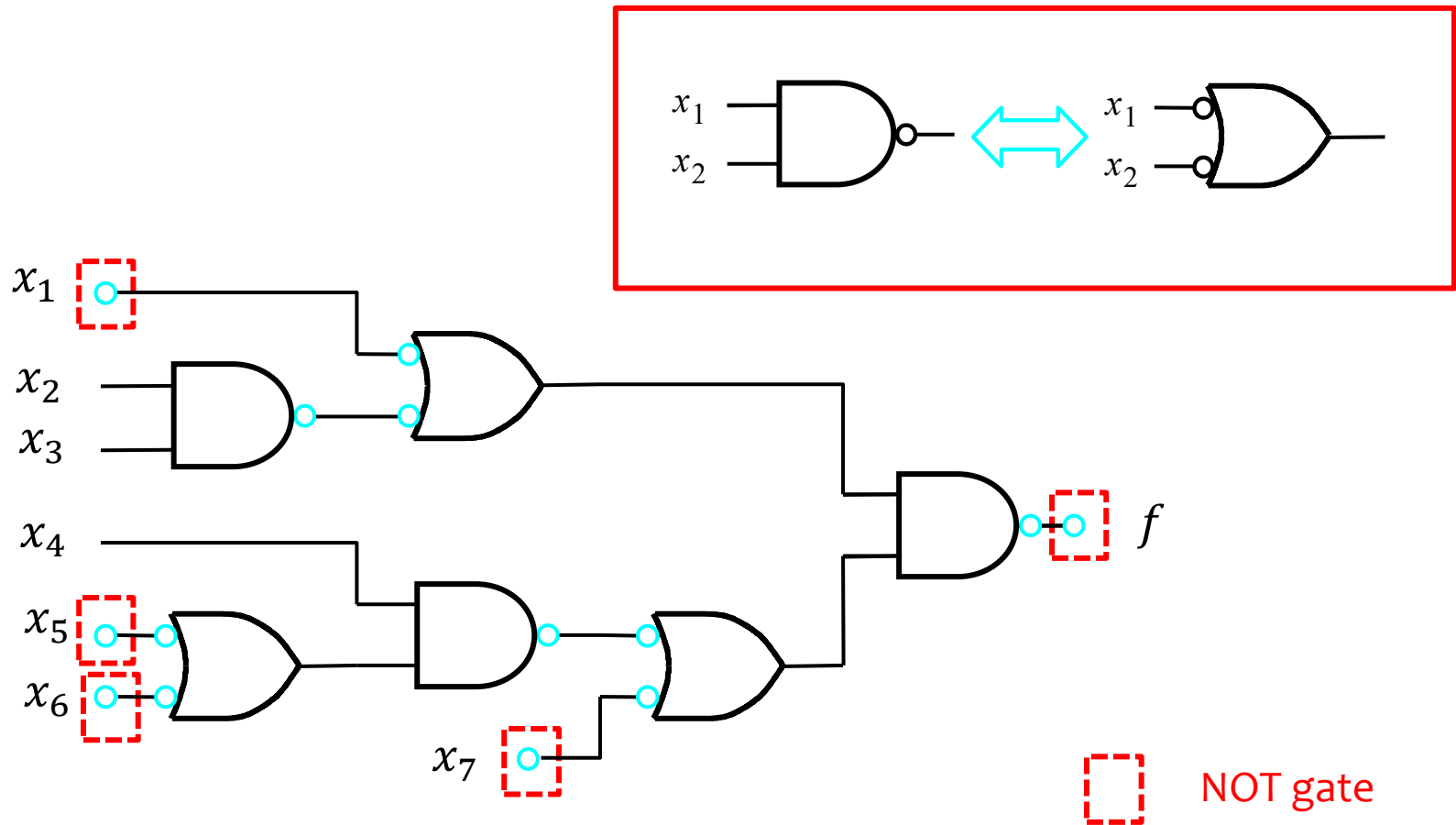

(b) Inversions needed to convert to NANDs

Figure 4.27. Conversion to a NAND-gate circuit.



○ ○ Multilevel NAND and NOR Circuits ○ ○

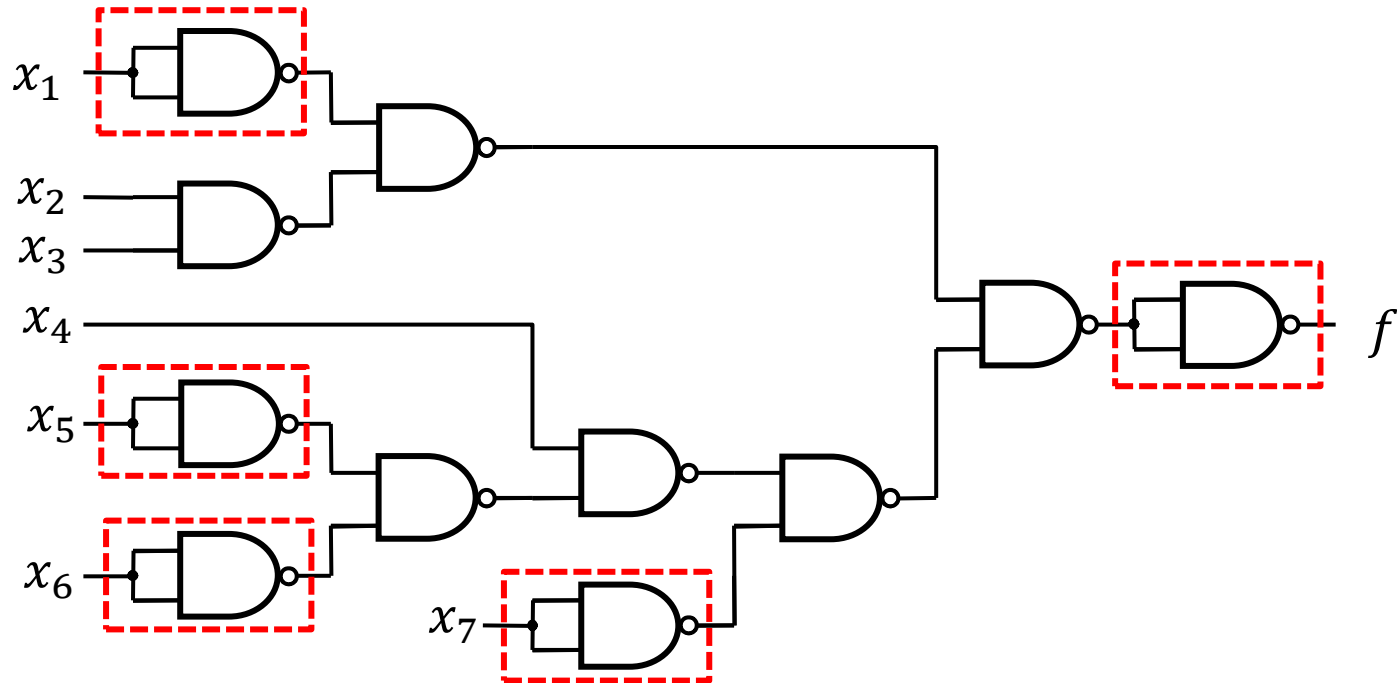

(c) NAND-gate circuit

Figure 4.27. Conversion to a NAND-gate circuit.

Multilevel NAND and NOR Circuits

  


 NOT gate

(a) Inversions needed to convert to NORs

Figure 4.28. Conversion to a NOR-gate circuit.

Multilevel NAND and NOR Circuits

 

(b) NOR-gate circuit


Figure 4.28. Conversion to a NOR-gate circuit.



ANALYSIS OF MULTILEVEL CIRCUITS



○○ Analysis of Multilevel Circuits ○○

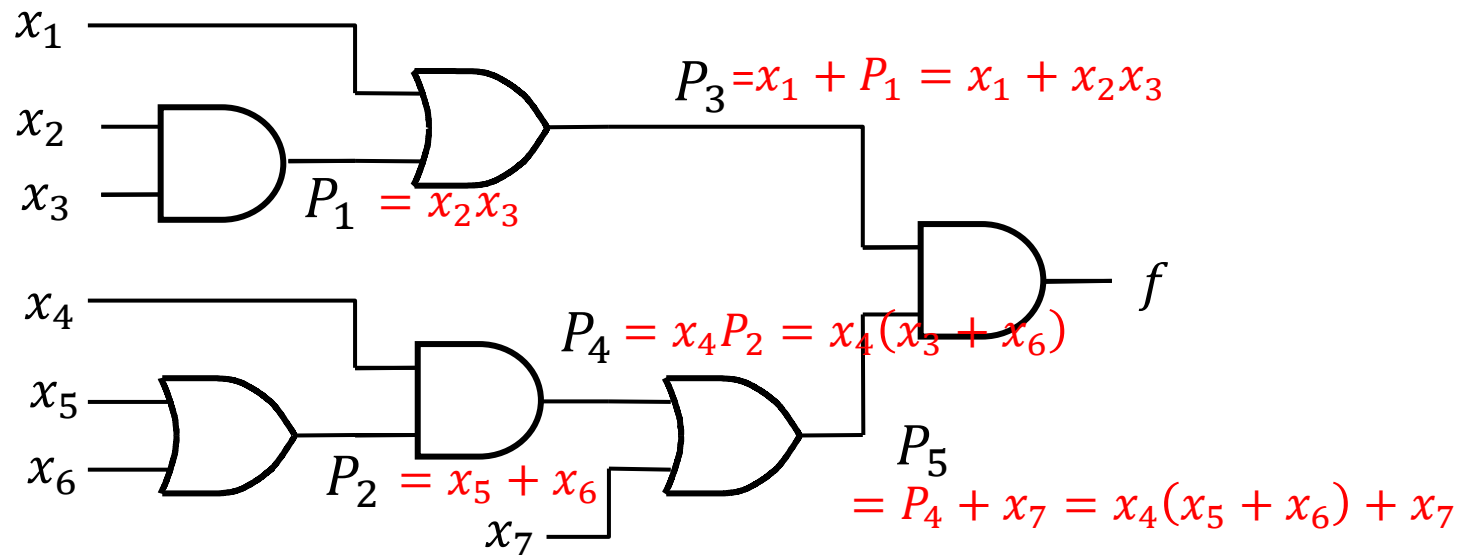

$$f = P_3 P_5 = (x_1 + x_2 x_3)(x_4(x_5 + x_6) + x_7)$$

$$= x_1 x_4 x_5 + x_1 x_4 x_6 + x_1 x_7 + x_2 x_3 x_4 x_5 + x_2 x_3 x_4 x_6 + x_2 x_3 x_7$$

Figure 4.29. Circuit for Example 4.10.



Summary



- ▶ Optimized logic circuits can be implemented by the **Karnaugh map**.
- ▶ **Don't care terms** in incompletely specified functions can be regarded by 0 or 1 for minimized logic function.
- ▶ **Multiple output** circuits can be efficiently implemented using the common units for multiple outputs.
- ▶ To solve **the fan-in problem**, output must be expressed in a form called a **multilevel logic** expression.
- ▶ Two important techniques for multilevel function are **factoring** and **functional decomposition**.

